

FH JOANNEUM
GRAZ

Model Based Design

02 Solar Cell

Training Unit 2 Solar Cell

Autor
David B. Heer

Lecturer
Alfred Steinhuber

Graz, January 8, 2019

Contents

1	Model Development	2
1.1	Parameters	2
1.2	Interface	3
1.3	Model Design	3
1.4	Simulation	6
2	Model Testing	7
2.1	Short Circuit	8
2.2	Open Circuit	8
2.3	Open Circuit with a higher Voltage	9
2.4	Open Circuit with a higher Irradiance	9
2.5	Storing of simulation results	10
2.6	Characteristic curves of the solar cell	11
3	Irradiance effect on solar cell performance	14
3.1	Temperature	14
3.2	Variable Irradiance	14
3.3	Maximum Power Point	17
4	Lookup table creation	21
5	Temperature Effect on PV Performance	22
	Literatur	25
	Abbildungen	25
	Tabellen	25
	Anhang	26
A	Matlab Code	26

Preparation

In the subject Model Based Design, a solar cell was modulated. The necessary equations are shown in Equation 1 - 4. The associated scheme is shown in Figure 1

$$I = P_{ph} - I_D - I_{sh} \quad (1)$$

$$I_{ph} = J_{sc} * A * \frac{G}{G_n} \quad (2)$$

$$I_D = I_0 * \left(e^{\frac{V + I * R_s}{m * V_T}} - 1 \right) \quad (3)$$

$$I_{sh} = \frac{V + I * R_s}{R_{sh}} \quad (4)$$

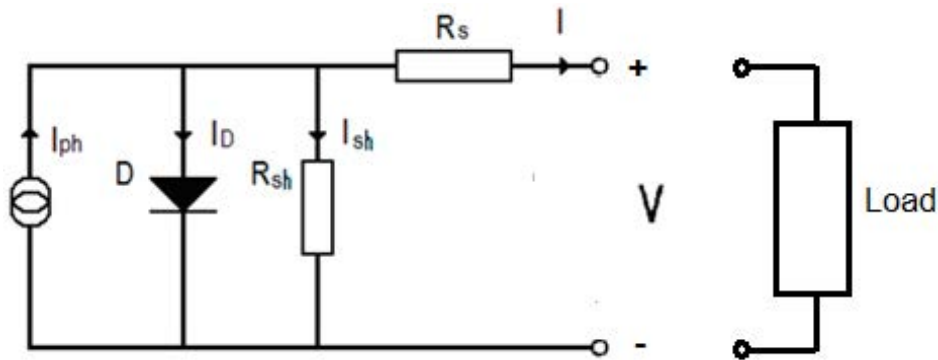


Figure 1: Scheme of solar cell with current source, perfect diode, internal and load resistors.

1 Model Development

1.1 Parameters

A .mat file has the advantage that it saves just variables. If you want to call variables in a .m file the whole skrip has to be calculated. This can be noticeable with many variables. See code in Listing 1 Line 5-19.

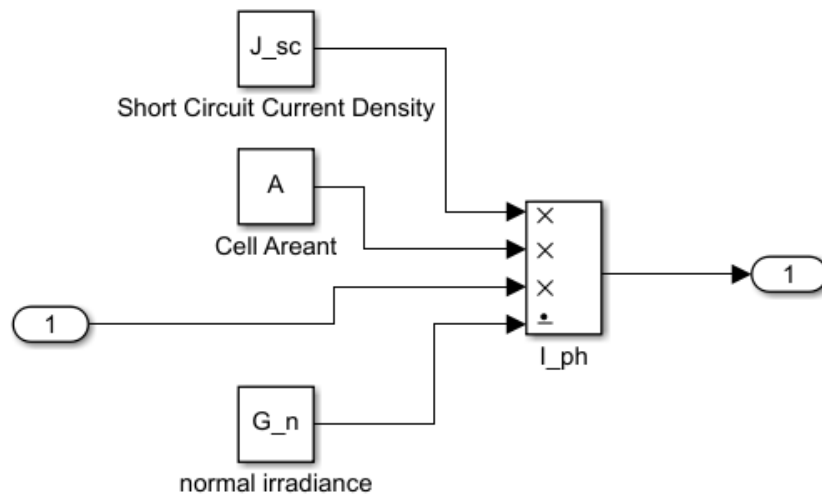


Figure 3: The total current of the irradiance without losses. The top block on Figure 2.

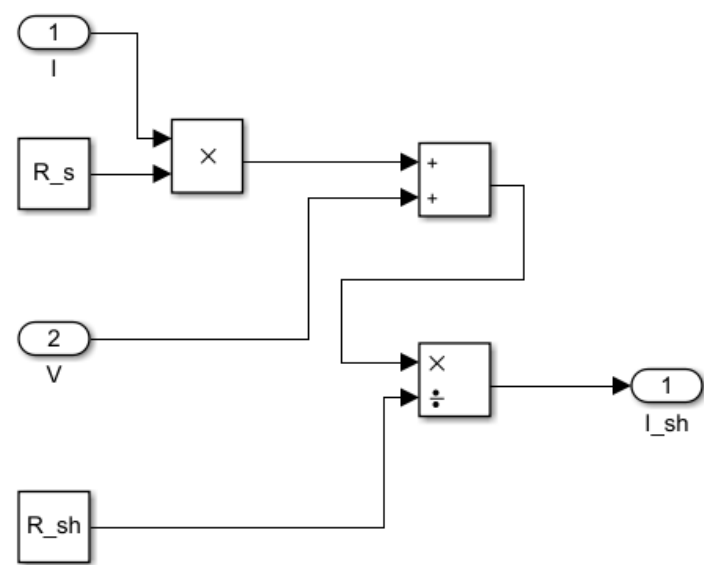


Figure 4: Loss current from the internal resistance. The block in the middle on Figure 2.

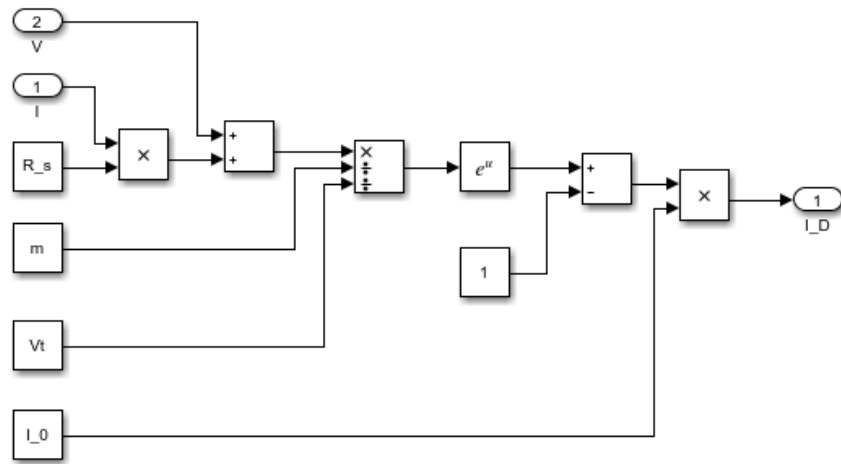


Figure 5: Loss current of the diode. The bottom block on [Figure 2](#)

1.4 Simulation

There were no warnings. Everything is fine.

2 Model Testing

For the following simulations the irradiance was fixed at $1000^W/m^2$. On all scopes the x-axes is the time in seconds. The y-axes are declared in each window.

2.1 Short Circuit

In the event of a short circuit, the output voltage is set to 0V. In Figure 6 are the graphs with the values visible. The total power is increased over the resistances R_s and R_{sh} . The current is visible on Figure 6 and is approximately 4.35A. A higher irradiance delivers a higher short circuit current. More about the influence of irradiance in Section 3.

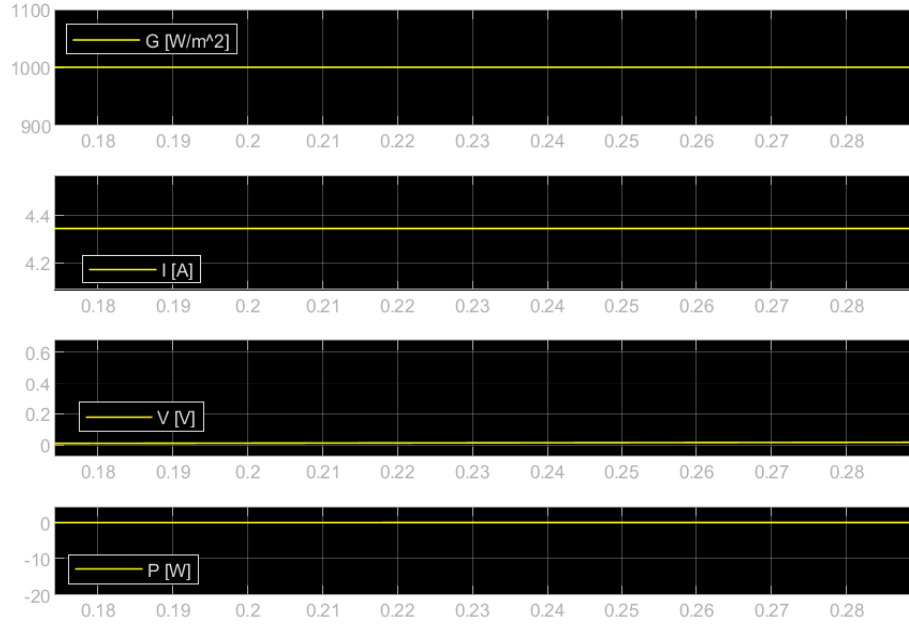


Figure 6: The scope around the point of a short circuit with irradiance of $1000 W/m^2$. On all scopes the x-axis is the time in seconds. The y-axis is declared in each window.

2.2 Open Circuit

When no load is connected, the whole power is increased over R_{sh} . The current I is 0A. The values can be read in Figure 7 at the place where the current crosses the 0A line. The voltage at this point is about 0.455V.

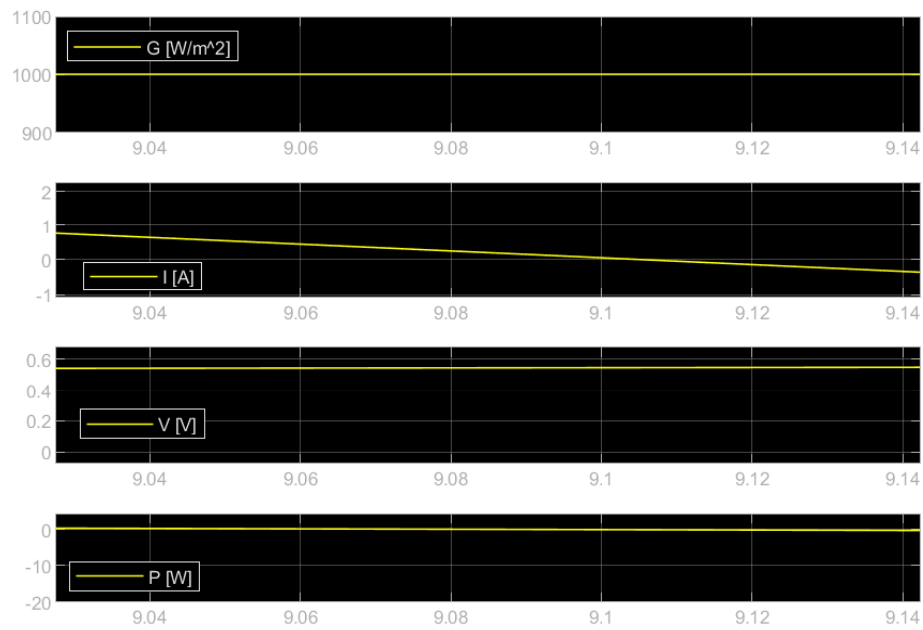


Figure 7: The scope around the point of an open circuit with irradiance of 1000 W/m^2 .

2.3 Open Circuit with a higher Voltage

If the voltage raises further the current get negative and the power too. That means the solar cell can't deliver more than this approximately 0.455 V by an irradiance of 1000 W/m^2 . This is visible in Figure 18.

2.4 Open Circuit with a higher Irradiance

If the irradiance is increased to 1500 W/m^2 , a higher output voltage will occur. This is visible on Figure 8 where the voltage is about 0.55 V . More about this topic in Section 3.

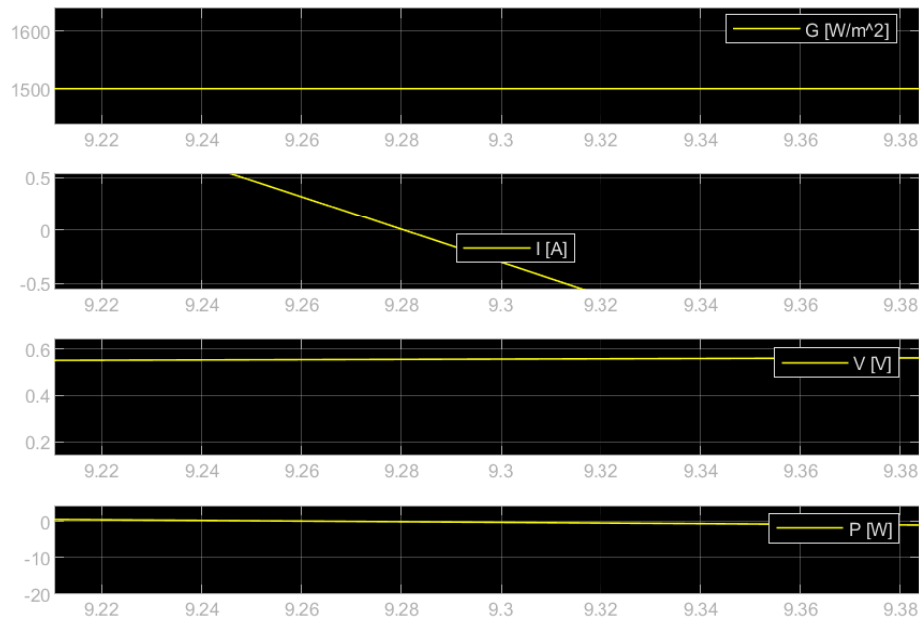


Figure 8: The scope around the point of an open circuit with irradiance of 1500 W/m^2 .

2.5 Storing of simulation results

The logged datas will be stored in a Struct. Each port has the properties:

- PortType
- PortIndex
- PropagatedName
- Blockpath
- Values
- Name

Each value is logged every 0.2 seconds. The Figure 9 is made with the logged datas after the resistance ramp was removed. The resistance and the power graphs are calculated with voltage and current. See Listing 1 Line 25-56.

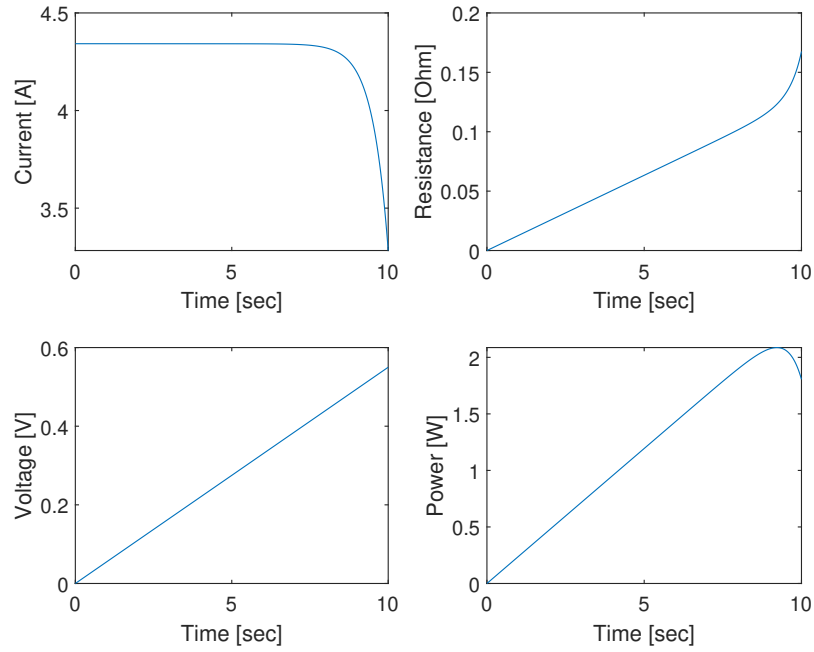


Figure 9: The plotted graph is made with the logged datas.

2.6 Characteristic curves of the solar cell

The simulink model (Figure 10) was extended with a variable R_{Load} as a ramp with a slope of $0.1\Omega/s$. The voltage V was defined as product of R_{Load} and I . The R_{Load} was added to the scope in Figure 11.

It is clear visible that the current becomes smaller after about one second with greater resistance and the voltage first rises quickly and goes to saturation at about 5.5V from about 1.25 seconds. The power has its peak of almost 2W at about 1.25 seconds.

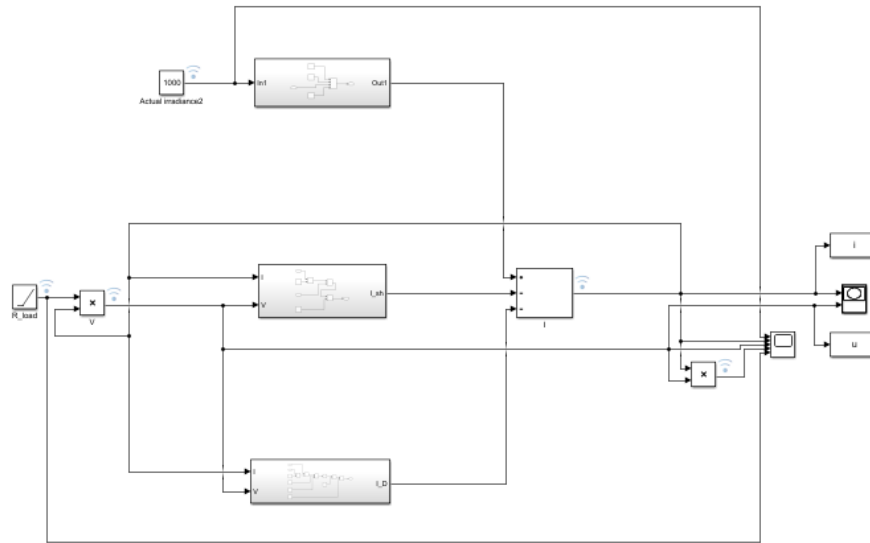


Figure 10: The voltage defined as product of I and R_{Load} . The variables V and I were recorded as array in Matlab. Visible on the right side of the figure, next to an XY-Scope.

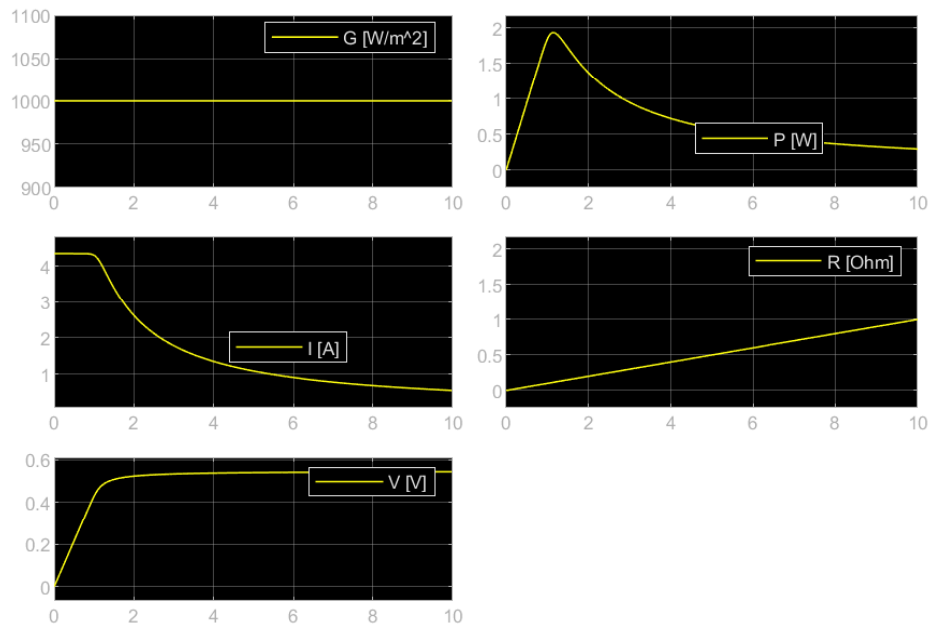


Figure 11: The extended scope with R_{Load} .

In Figure 12 is the dependence between current and voltage. The goal is to find the point with the largest area with the product of voltage and current. This can be seen more easily in Figure 11 as peak of the power in the graph top right.

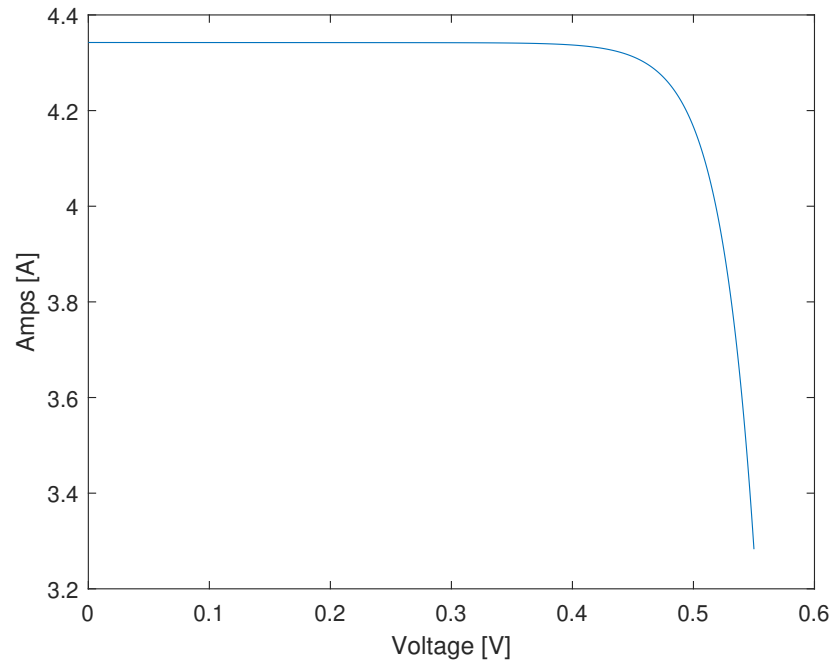


Figure 12: XY-Plot with voltage and current. The product of current and voltage from each point on the line is the resulting power in watt.

3 Irradiance effect on solar cell performance

3.1 Temperature

The thermal voltage was already set at the start of the laboratory unit to 25.85V at 300K. The difference of a ΔT of 1.85K is unknown. More on this topic in Section 5.

3.2 Variable Irradiance

On the following Figures 13 - 17 the irradiance was varied. All other settings have been retained. The scaling of the plots is also the same in all figures. On Figure 18 is an current voltage plot overview with all irradiances. On Figure 21 is an overview with power and voltage with different irradiances. The Matlab code for Figure 18 and Figure 21 is in Listing 1 Line 66 - 126.

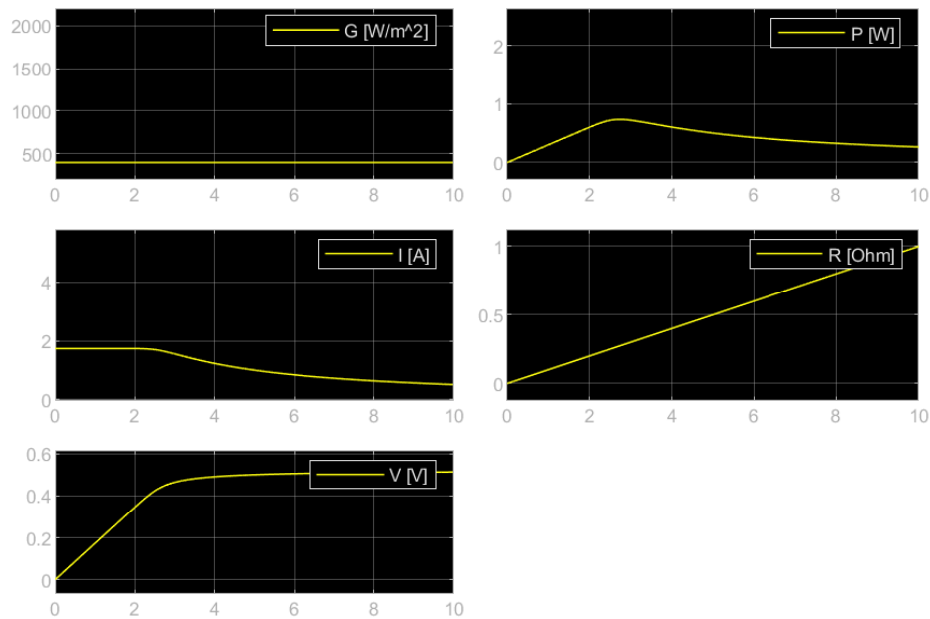


Figure 13: Fixed irradiance at 400 W/m^2 with a variable resistance as ramp from $0\text{-}1\Omega$

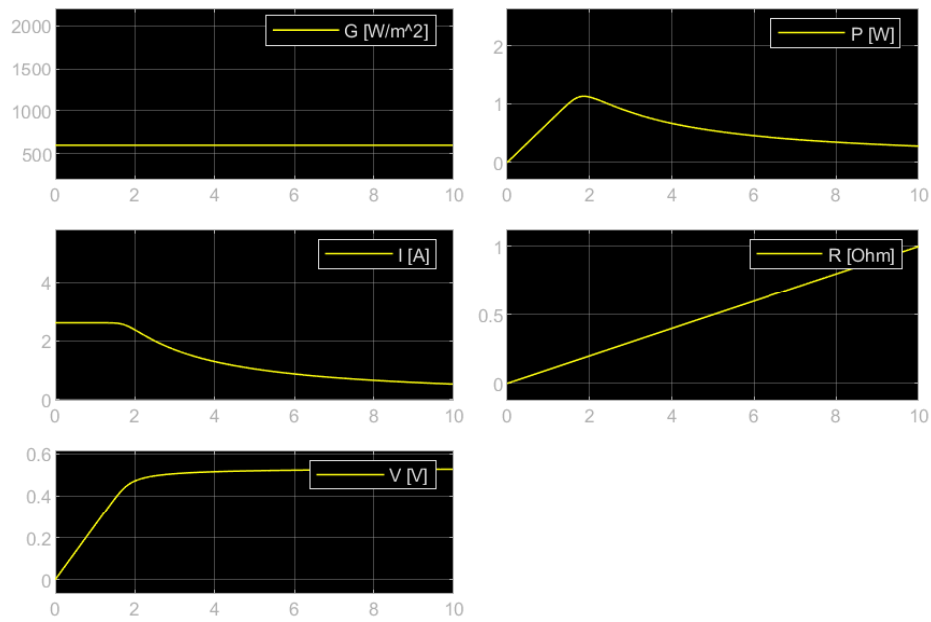


Figure 14: Fixed irradiance at $600 W/m^2$ with a variable resistance as ramp from $0-10 \Omega$

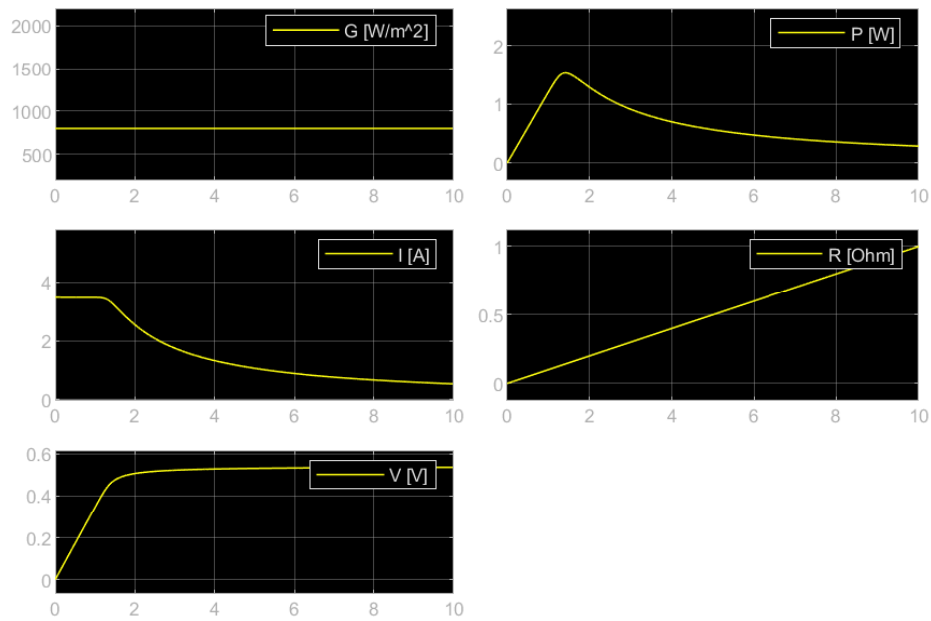


Figure 15: Fixed irradiance at $800 W/m^2$ with a variable resistance as ramp from $0-10 \Omega$

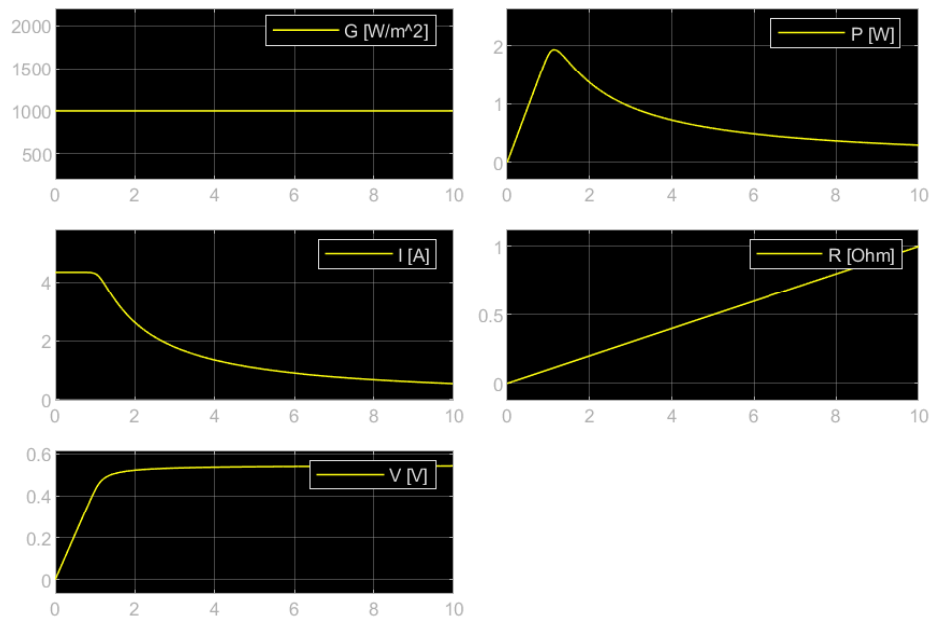


Figure 16: Fixed irradiance at 1000 W/m^2 with a variable resistance as ramp from $0\text{-}10\Omega$

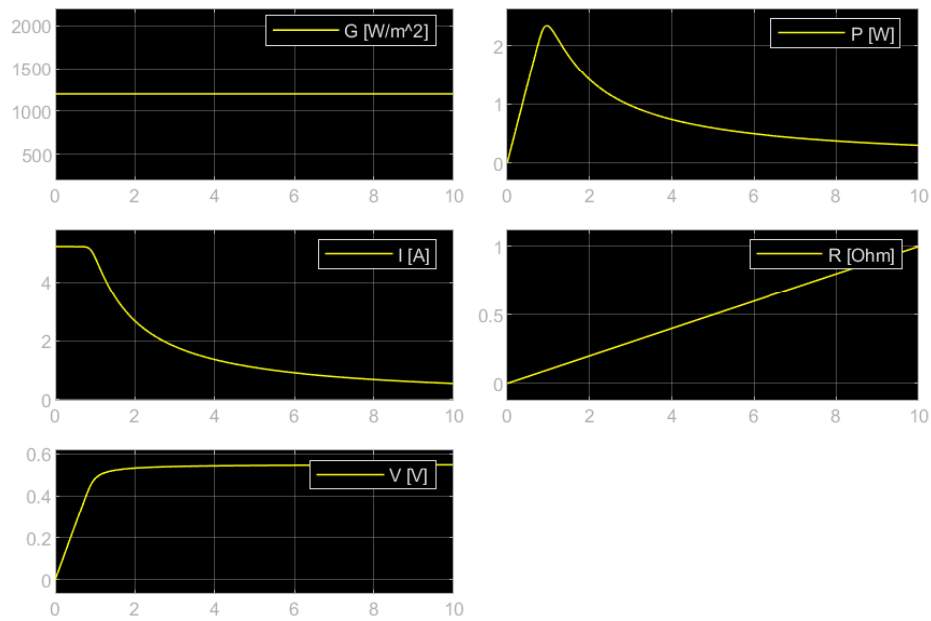


Figure 17: Fixed irradiance at 1200 W/m^2 with a variable resistance as ramp from $0\text{-}10\Omega$

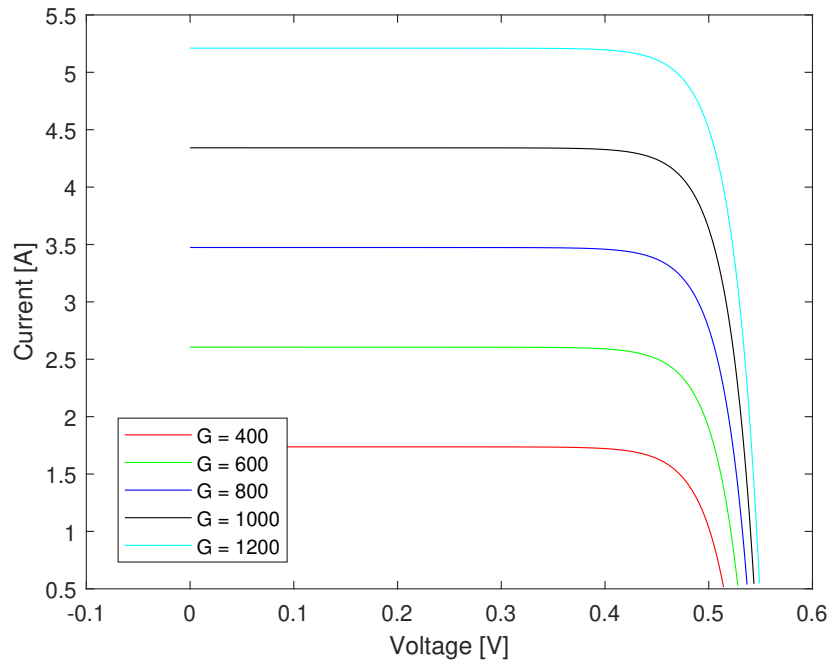


Figure 18: Current dipence on voltage. The different lines symbolizes different irradiances G .

3.3 Maximum Power Point

On the following Figures 19 and 20 are an XY-plot of current and voltage next to a XY-plot of voltage and power. The scale is different on each plot to make the Maximum Power Point better visible. On the last Figure 21 is an overview of all Maximum Power Points from the different irradiances. The Matlab code is in Listing 1 Line131 - 145.

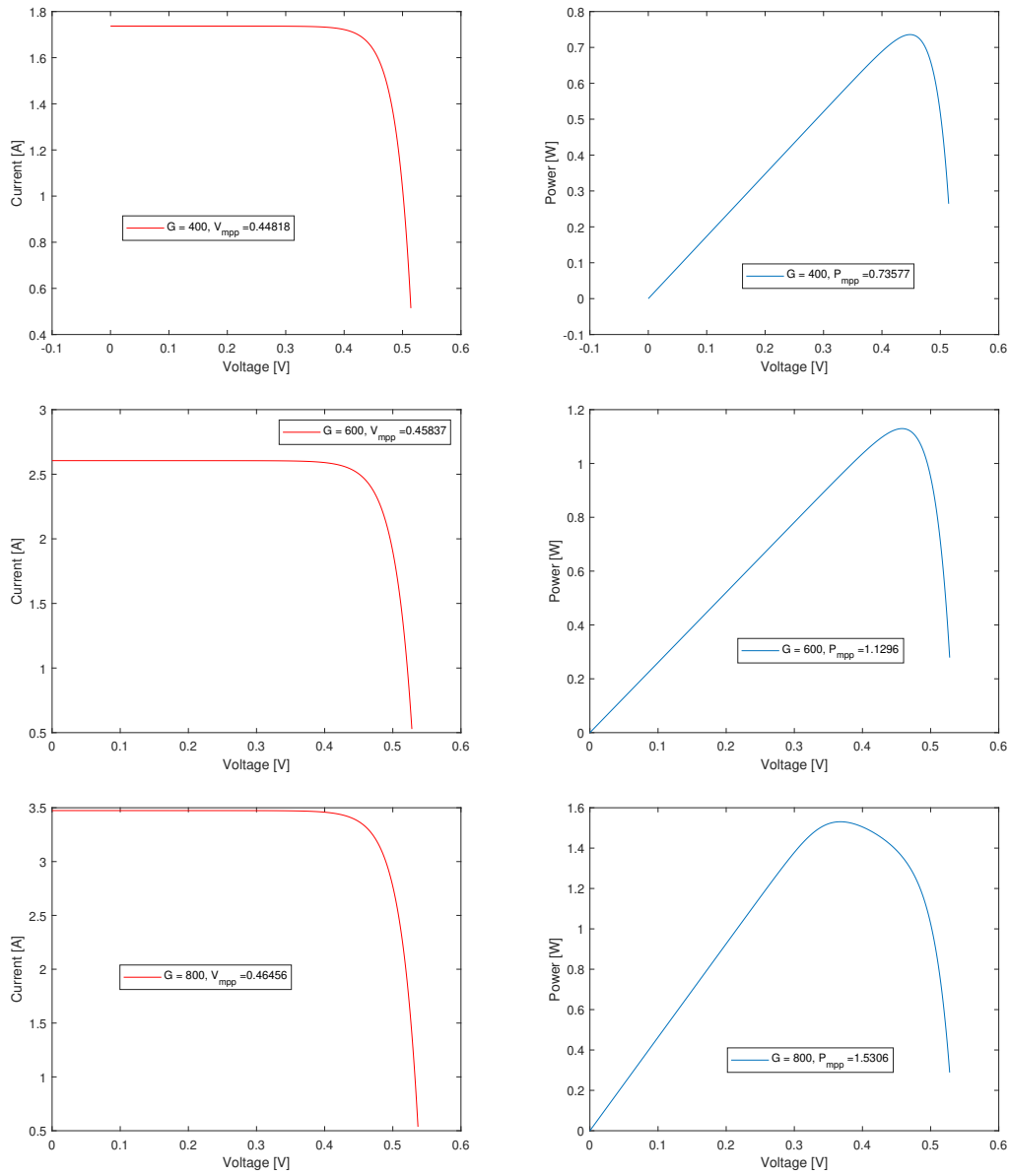


Figure 19: Maximum Power Point, $G = 400, 600, 800$
1 of 2

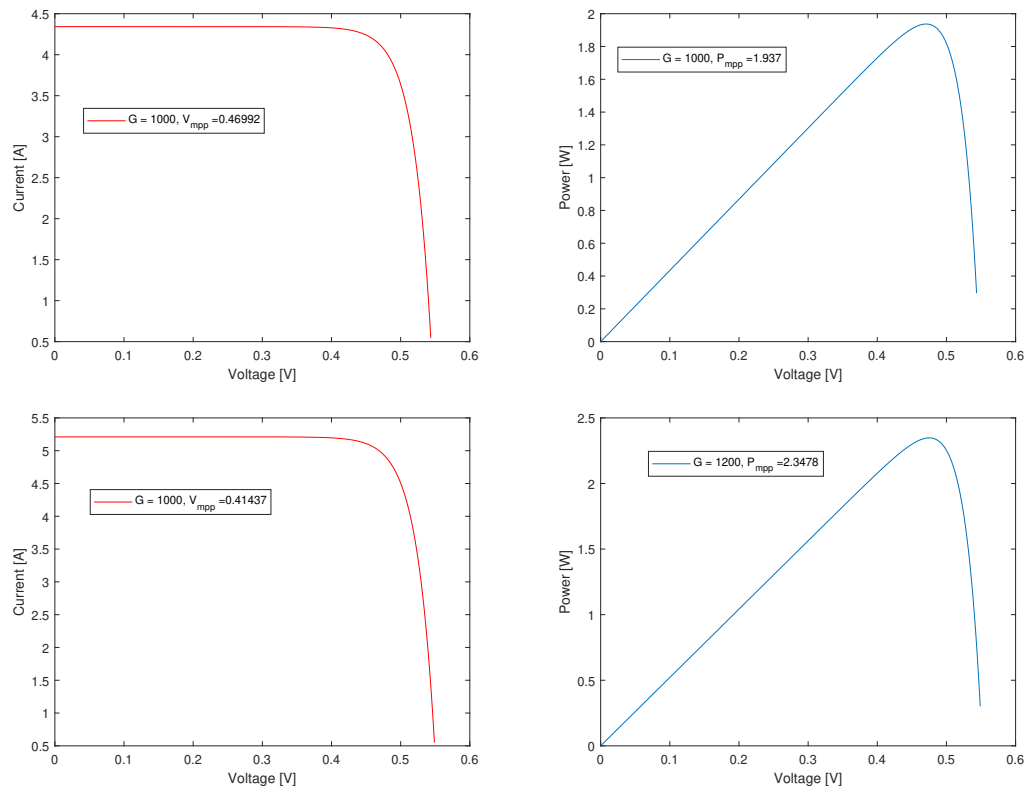


Figure 20: Maximum Power Point, $G = 1000, 1200$
2 of 2

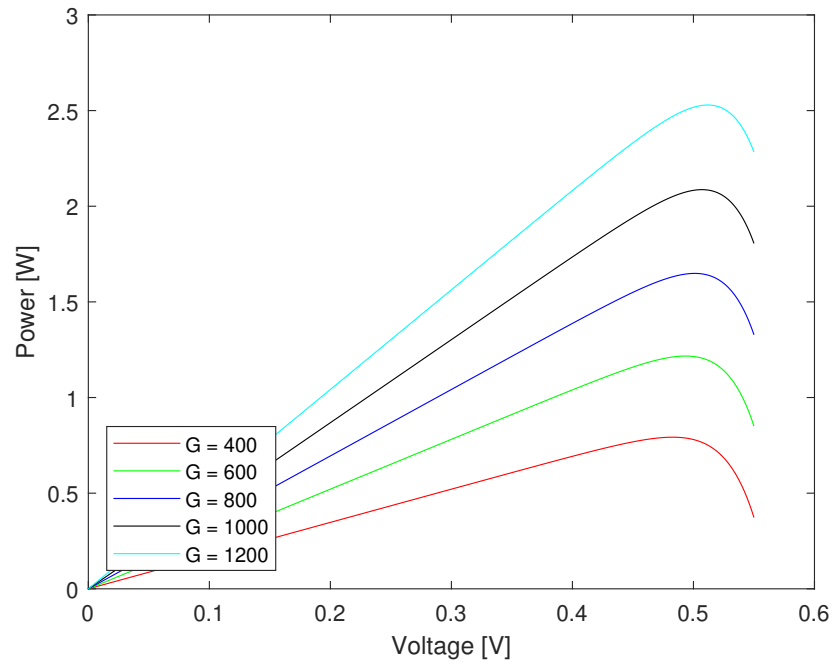


Figure 21: Power dependence on voltage. The different lines symbolizes different irradiances G .

4 Lookup table creation

In the Tables 1 and 2 are two examples of lookup tables. Table 1 is two dimensional with two inputs. Table 2 is like in the task with voltage as input and current as output. This lookup tables are just for visualisation. So there are less values in it. The code to built these two Arrays is in Listing 1 Line 148 - 180.

With the commad tic and toc would be stoped the simulation time from the code in Listing 1 Line 64 - 97. The stoped time was 6.9 seconds. The model was simulated five times with different irradiances. The average for each simulation is so $\frac{6.9s}{5} = 1.4s$.

The next step was to comment out the saves to the arrays and measure the time again. This total time was 6.6s. Thats 1.3s per simulation. Not a big difference to the preview time.

Finally, the time was measured to read the array. The result was 0.03s and much smaller then one simulation run. The measurements are not very meaningful and are difficult to reproduce.

The advantage is that if the data is often needed, the simulation does not always have to be restarted. Thats saves time and energy. This is helpful in simulations which often have to be repeated.

	0Ω	$40m\Omega$	$80m\Omega$	$120m\Omega$	$160m\Omega$	$200m\Omega$	$240m\Omega$	$280m\Omega$
$400W/m^2$	0	0.1207	0.2413	0.3619	0.4825	0.6018	0.7049	0.7347
$600W/m^2$	0	0.2715	0.543	0.8141	1.0657	1.1161	1.015	0.9055
$800W/m^2$	0	0.4827	0.9652	1.427	1.4834	1.2872	1.1107	0.971
$1000W/m^2$	0	0.7542	1.5069	1.9265	1.6412	1.3686	1.1648	1.0114
$1200W/m^2$	0	1.086	2.1503	2.1538	1.7291	1.4216	1.2026	1.0407

Table 1: Lookup Table with G and R_{Load} as input and P as output

Voltage [V]	0	0.022	0.044	0.066	0.088	0.11	0.132	0.154
Current [A]	4.3424	4.3424	4.3423	4.3423	4.3423	4.3423	4.3422	4.3422

Table 2: Lookup Table with G and R_{Load} as input and P as output

5 Temperature Effect on PV Performance

In this section, the influence of temperature was included. For this purpose, the simulink model was adjusted as shown in Figure 22. The model was simulated with the temperatures 15°C, 20°C, 30°C, 40°C and 50°C. The values were converted from Celsius to Kelvin for the Input. The code is in Listing 1 Line 186 - 241.

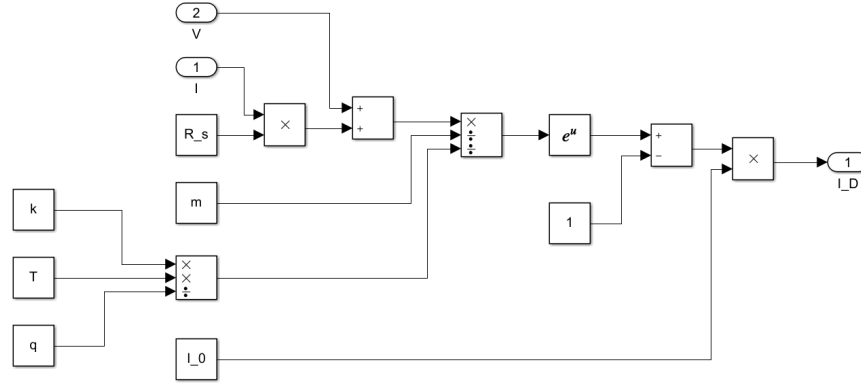


Figure 22: Update of the Figure 5. Now with the influence of temperature.

In Figure 23 and 24 are the plots with current and power depending on the voltage at different temperatures. Mathematically, it is true that the output power increases with higher temperature. Because V_t gets bigger with increasing temperature T .

$$T_t = \frac{k * T}{q} \quad (5)$$

The larger V_t effects that the loss current become smaller. This can be seen in Equation 3. The plots prove this calculation, seen in Figure 23 and 24. On this figures is also visible that that the influence is only visible with a large R_{load} . However, this is not what can be expected physicaly. Solar cells produces more energy by lower temperatures [1] [2].

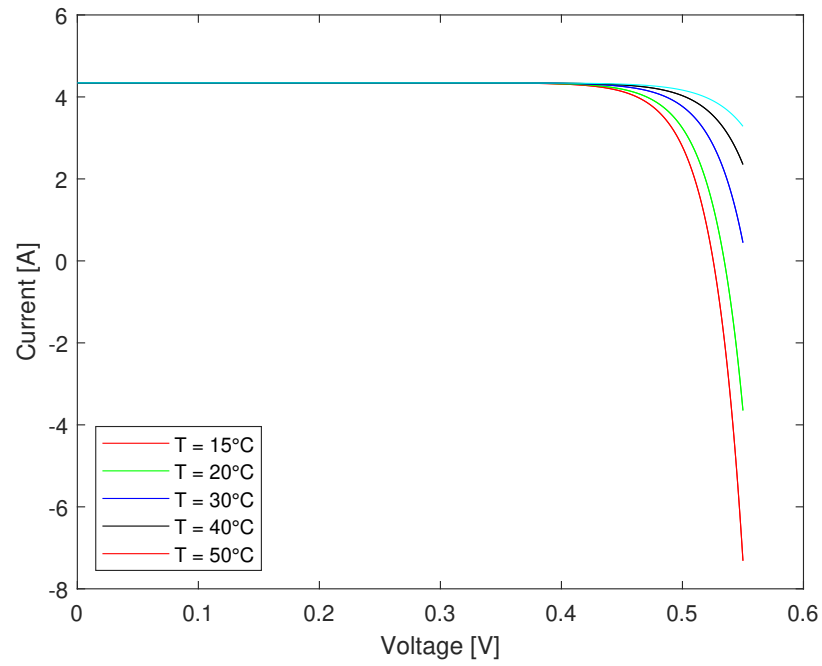


Figure 23: Current dipence on Voltage with a constant irradiancie. The different lines are the different temperatures 15°C, 20°C, 30°C, 40°C and 50°C.

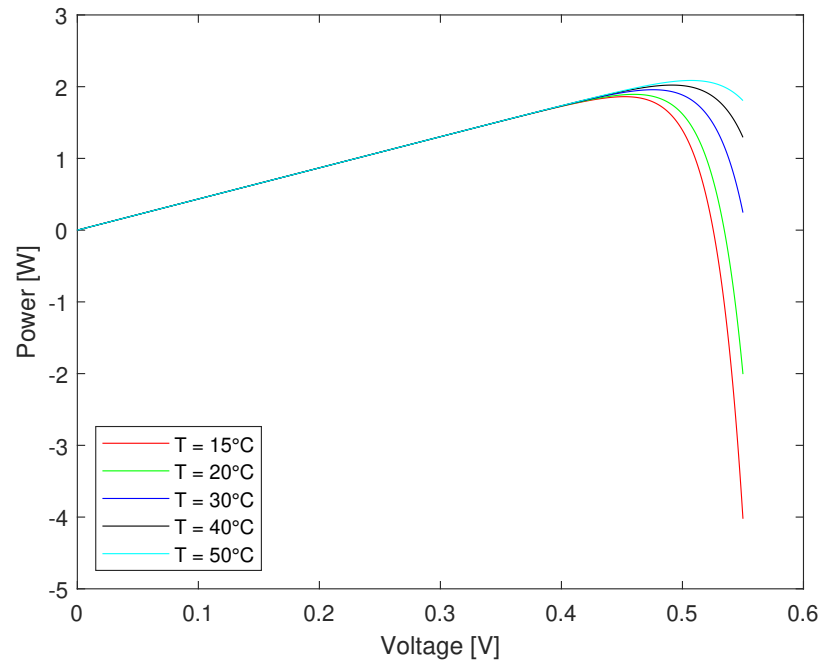


Figure 24: Power dipence on Voltage with a constant irradiance. The different lines are the different temperatures 15°C, 20°C, 30°C, 40°C and 50°C.

References

- [1] U. Tietze, C. Schenk, and E. Gamm, *Halbleiter-Schaltungstechnik (German Edition)*. Springer, 2012.
- [2] A. Niederl, “Leistungssteigerung von Photovoltaikanlagen durch Modulkühlung.” Website. Online available on: https://www.tugraz.at/fileadmin/user_upload/Events/Eninnov2014/files/lf/LF_Niederl.pdf ; called on 30. October 2018.

List of Figures

1	Scheme of solar cell	2
2	Mathematical overview scheme based on the Equations 1 - 4	3
3	The total current of the irradiance without losses.	4
4	Loss current from the internal resistance.	5
5	Loss current of the diode.	6
6	The scope around the point of a short circuit with irradiance of 1000 W/m^2	8
7	The scope around the point of an open circuit with irradiance of 1000 W/m^2	9
8	The scope around the point of an open circuit with irradiance of 1500 W/m^2	10
9	The plotted graph is made with the logged datas.	11
10	The voltage defined as product of I and R_{Load}	12
11	The extended scope with R_{Load}	12
12	XY-Plot with voltage and current. The product of current and voltage from each point on the line is the resulting power in watt.	13
13	Fixed irradiance at 400 W/m^2 with a variable resistance as ramp from $0-1\Omega$	14
14	Fixed irradiance at 600 W/m^2 with a variable resistance as ramp from $0-1\Omega$	15
15	Fixed irradiance at 800 W/m^2 with a variable resistance as ramp from $0-1\Omega$	15
16	Fixed irradiance at 1000 W/m^2 with a variable resistance as ramp from $0-1\Omega$	16
17	Fixed irradiance at 1200 W/m^2 with a variable resistance as ramp from $0-1\Omega$	16
18	Current dipence on voltage.	17
19	Maximum Power Point, $G = 400, 600, 800$ 1 of 2	18
20	Maximum Power Point, $G = 1000, 1200$ 2 of 2	19
21	Power dipence on voltage. The different lines symbolizes different irradiances G.	20
22	Update of the Figure 5. Now with the influence of temperature.	22
23	Current dipence on Voltage with a constant irradiance and different temperatures	23
24	Power dipence on Voltage with a constant irradiance.	24

List of Tables

1	Lookup Table with G and R_{Load} as input and P as output	21
2	Lookup Table with G and R_{Load} as input and P as output	21

Anhang

A Matlab Code

Listing 1: Matlabcode

```

1      % Variables for MBD Unit2
2      %1.1
3      clear all;
4
5      J_sc = 343;      %A/m2
6      G = 1000;      %W/m2
7      G_n = 1000;      %W/m2
8      A = 0.01266;      %m2
9      R_s = 1e-6;      %Ohm
10     R_sh = 1000;      %Ohm
11     I_0 = 2.8e-9;      %A
12     Vt = 25.85e-3;      %V
13     m = 1;      % 1= ideal diode
14     V = 0.5;      %V
15     k= 1.38064852*10^-23;
16     T = 26.85 +273.15;
17     q=1.602176565*10^-19;
18
19     save var.mat;
20
21     %%
22     % Logdaten auslesen
23     % logkout{2}.Values.Data
24     % 2.4
25     figure(99)
26     subplot(2,2,1);
27     plot(logkout{2}.Values.Time, logkout{2}.Values.Data)
28     xlabel('Time_[sec]')
29     ylabel('Current_[A]')
30
31     subplot(2,2,2);
32     plot(logkout{2}.Values.Time, logkout{4}.Values.Data ./logkout{2}.Values.
        Data)
33     xlabel('Time_[sec]')
34     ylabel('Resistance_[Ohm]')
35
36     subplot(2,2,3);
37     plot(logkout{2}.Values.Time, logkout{4}.Values.Data)
38     xlabel('Time_[sec]')
39     ylabel('Voltage_[V]')
40
41     subplot(2,2,4);
42     plot(logkout{2}.Values.Time, logkout{3}.Values.Data)

```

```

43     xlabel('Time_[sec]')
44     ylabel('Power_[W]')
45
46     %saveas(gcf, '../..//documentation/figures/subplots.eps', 'eps')
47
48     %%
49     % XY Plot with u & i
50     % 2.4
51     sim('unit2');
52     x=u.get('Data');
53     y=i.get('Data');
54     plot(x,y);
55     xlabel('Voltage_[V]')
56     ylabel('Amps_[A]')
57
58
59     %%
60     %sim('unit2', 'G', [400, 600,800,1000,1200])
61     % Simuliere mit verschiedenen G-Werten und speichere die Werte
62     % Sim Zeit nehmen mit tic - toc
63     % 3.1 & 4
64     tic
65
66     G = 400;
67     sim('unit2');
68     u400=u.get('Data');
69     i400=i.get('Data');
70
71     G = 600;
72     sim('unit2');
73     u600=u.get('Data');
74     i600=i.get('Data');
75
76     G = 800;
77     sim('unit2');
78     u800=u.get('Data');
79     i800=i.get('Data');
80
81     G = 1000;
82     sim('unit2');
83     u1000=u.get('Data');
84     i1000=i.get('Data');
85
86     G = 1200;
87     sim('unit2');
88     u1200=u.get('Data');
89     i1200=i.get('Data');
90
91     toc
92
93     %%

```

```

94     % Zeit um Array zu lesen
95     tic
96     [P_max, max_ind] = max(u1200.*i1200)
97     toc
98
99     %%
100    %XY Plot Leistung über Spannung
101    % 3.2
102    plot(u400, i400.*u400, 'r')
103    hold on
104    xlabel('Voltage_[V]');
105    ylabel('Power_[W]');
106    plot(u600, i600.*u600, 'g')
107    plot(u800, i800.*u800, 'b')
108    plot(u1000, i1000.*u1000, 'k')
109    plot(u1200, i1200.*u1200, 'c')
110    legend({'G_=_400', 'G_=_600', 'G_=_800', 'G_=_1000', 'G_=_1200'}, 'Location'
           , 'southwest')
111    hold off
112    %saveas(gcf, '../..//documentation/figures/xy_vp.eps', 'eps')
113
114    %%
115    %XY Plot Strom über Spannung
116    % 3.2
117    plot(u400, i400, 'r')
118    hold on
119    xlabel('Voltage_[V]');
120    ylabel('Current_[A]');
121    plot(u600, i600, 'g')
122    plot(u800, i800, 'b')
123    plot(u1000, i1000, 'k')
124    plot(u1200, i1200, 'c')
125    legend({'G_=_400', 'G_=_600', 'G_=_800', 'G_=_1000', 'G_=_1200'}, 'Location'
           , 'southwest')
126    hold off
127    %saveas(gcf, '../..//documentation/figures/xy_vc.eps', 'eps')
128
129    %%
130    % XY Plot mit den max values in der Legende
131    [P_value, index_peak] = max(u1000.*i1000);
132    figure(3);
133    plot(u1200, i1200, 'r')
134    xlabel('Voltage_[V]');
135    ylabel('Current_[A]');
136    legend(strcat('G_=_1000, V_{mpp}_=_', num2str(u1000(index_peak))));
137
138    %%
139    % XY Plot mit den max values in der Legende
140    % 3.3
141    figure(2);
142    plot(u1200, u1000.*i1000);

```

```

143 xlabel('Voltage_[V]');
144 ylabel('Power_[W]');
145 legend(strcat('G_=_1200,_P_{mpp}_=_', num2str(P_value)));
146
147 %%
148 %%Erstelle die Arrays zur Visualisierung für die Lookuptables mit
    undersampling
149 % 4.0
150 % ilarr = i1.get('Data');
151 % u2arr = u1.get('Data');
152 %
153 % c2 = 1;
154 % for c = 1:8
155 %     p400(c) = u400(c2) * i400(c2);
156 %     p600(c) = u600(c2) * i600(c2);
157 %     p800(c) = u800(c2) * i800(c2);
158 %     p1000(c) = u1000(c2) * i1000(c2);
159 %     p1200(c) = u1200(c2) * i1200(c2);
160 %     c2 = c2 + 40;
161 % end
162
163 % for c = 1:1000
164 %     iv(c) = ilarr(c2);
165 %     uv(c) = u2arr(c2);
166 %     c2 = c2 + 1;
167 % end
168 %
169 % plt = [p400; p600; p800; p1000; p1200];
170 % plt2 = [iv; uv];
171 % toc
172 % figure(4);
173 % plot(uv, iv);
174 % xlabel('Voltage [V]');
175 % ylabel('Ampere [A]');
176 % legend();
177 % toc
178 %%Erstelle den Sourcecode der Arrays für LaTeX
179 %latexable = latex(sym(vpa(round(plt2, 4))))
180 %latexable = latex(sym(vpa(round(plt, 4))))
181
182 %%
183 % Simulation mit verschiedenen Temperaturen
184 % 5.2
185
186 T = 15 + 273.15;
187 sim('unit2');
188 u15=u.get('Data');
189 i15=i.get('Data');
190
191 T = 20 + 273.15;
192 sim('unit2');

```

```

193     u20=u.get('Data');
194     i20=i.get('Data');
195
196     T = 30 + 273.15;
197     sim('unit2');
198     u30=u.get('Data');
199     i30=i.get('Data');
200
201     T = 40 + 273.15;
202     sim('unit2');
203     u40=u.get('Data');
204     i40=i.get('Data');
205
206     T = 50 + 273.15;
207     sim('unit2');
208     u50=u.get('Data');
209     i50=i.get('Data');
210
211
212     %%
213     %XY Plot Leistung über Voltage
214     % 5.3
215     plot(u15(1:end), i15(1:end).*u15(1:end), 'r')
216     hold on
217     xlabel('Voltage_[V]');
218     ylabel('Power_[W]');
219     plot(u20(1:end), i20(1:end).*u20(1:end), 'g')
220     plot(u30(1:end), i30(1:end).*u30(1:end), 'b')
221     plot(u40(1:end), i40(1:end).*u40(1:end), 'k')
222     plot(u50(1:end), i50(1:end).*u50(1:end), 'c')
223
224     legend({'T_=_15C', 'T_=_20C', 'T_=_30C', 'T_=_40C', 'T_=_50C'}, 'Location', 'southwest')
225     hold off
226     %saveas(gcf, '../..//documentation/figures/xy_vp_t.eps', 'eps')
227
228     %%
229     %XY Plot Strom über Spannung
230     % 5.3
231     plot(u15(1:end), i15(1:end), 'r')
232     hold on
233     xlabel('Voltage_[V]');
234     ylabel('Current_[A]');
235     plot(u20(1:end), i20(1:end), 'g')
236     plot(u30(1:end), i30(1:end), 'b')
237     plot(u40(1:end), i40(1:end), 'k')
238     plot(u50(1:end), i50(1:end), 'c')
239     legend({'T_=_15C', 'T_=_20C', 'T_=_30C', 'T_=_40C', 'T_=_50C'}, 'Location', 'southwest')
240     hold off
241     %saveas(gcf, '../..//documentation/figures/xy_vc_t.eps', 'eps')

```